


Lab Assignment 4

Question 1

Verilog Code

```
1 module half_adder(  
2     output S,C,  
3     input A,B);  
4  
5     xor(S,A,B);  
6     and(C,A,B);  
7  
8 endmodule  
9
```

Quatrus Prime Waveform

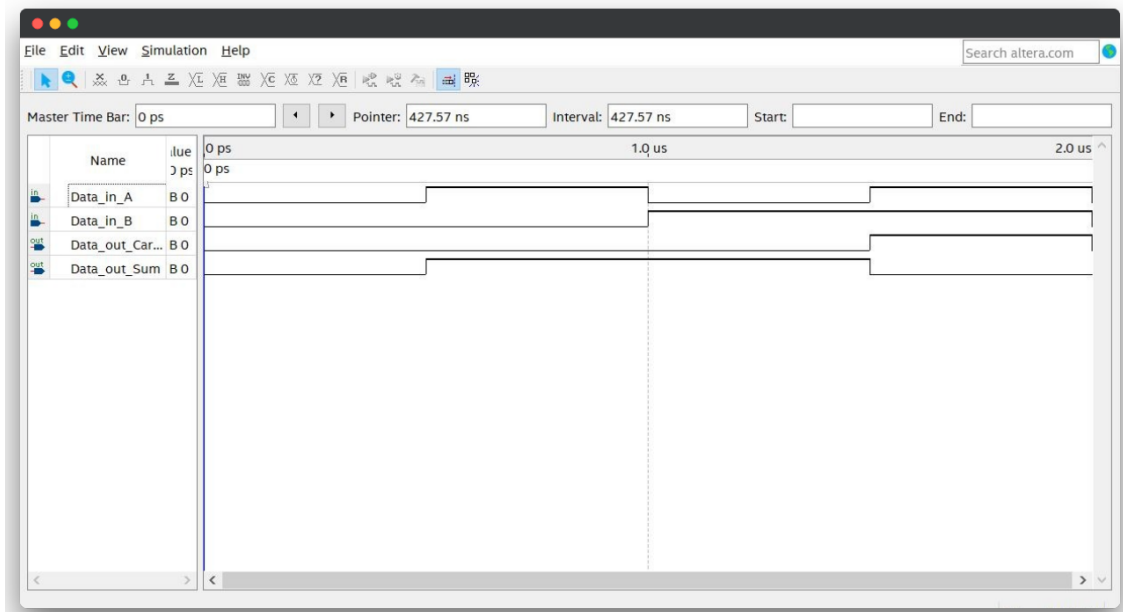


Question 2

Verilog Code

```
1 module twos(a1, a2, a3, a4, o1, o2, o3, o4);
2
3     input a1, a2, a3, a4;
4     output o1, o2, o3, o4;
5     wire c1, c2, c3, c4;
6     assign c0 = 1;
7     half_adder ha1(.a(~a1), .b(c0), .sum(o1), .carry(c1));
8     half_adder ha2(.a(~a2), .b(c1), .sum(o2), .carry(c2));
9     half_adder ha3(.a(~a3), .b(c2), .sum(o3), .carry(c3));
10    half_adder ha4(.a(~a4), .b(c3), .sum(o4), .carry(c4));
11
12 endmodule
13
```

Quatrus Prime Waveform

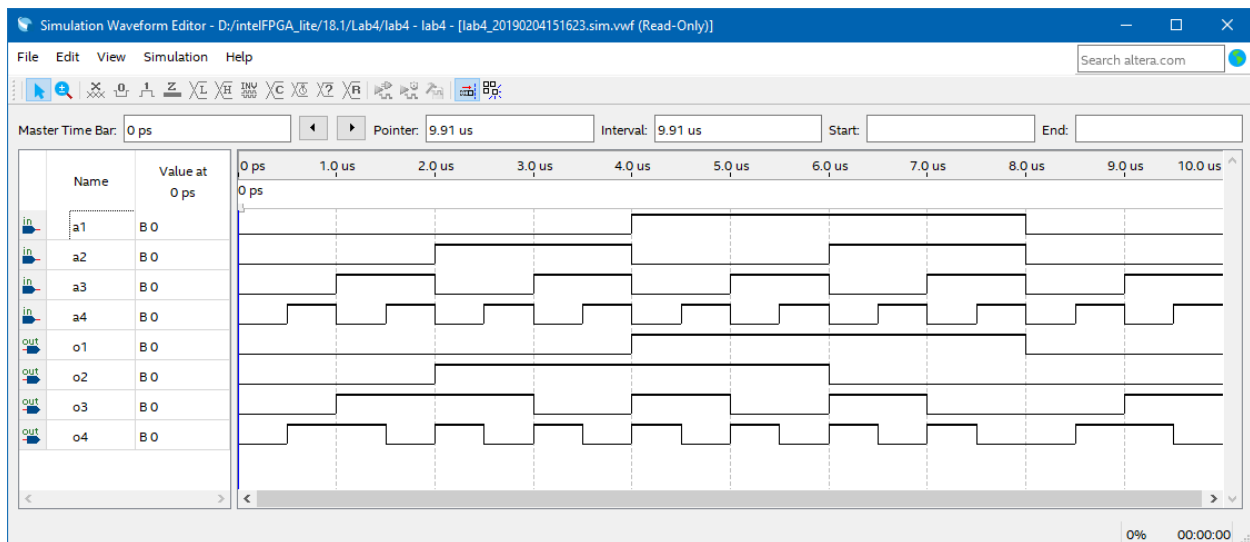


Question 3

Verilog Code

```
1 module full_adder(  
2     Data_in_A, //input A  
3     Data_in_B, //input B  
4     Data_in_C, //input C  
5     Data_out_Sum,  
6     Data_out_Carry  
7 );  
8  
9     input Data_in_A;  
10    input Data_in_B;  
11    input Data_in_C;  
12    output Data_out_Sum;  
13    output Data_out_Carry;  
14  
15    wire ha1_sum;  
16    wire ha2_sum;  
17    wire ha1_carry;  
18    wire ha2_carry;  
19    wire Data_out_Sum;  
20    wire Data_out_Carry;  
21  
22    half_adder ha1(  
23        .Data_in_A(Data_in_A),  
24        .Data_in_B(Data_in_B),  
25        .Data_out_Sum(ha1_sum),  
26        .Data_out_Carry(ha1_carry)  
27    );  
28  
29    half_adder ha2(  
30        .Data_in_A(Data_in_C),  
31        .Data_in_B(ha1_sum),  
32        .Data_out_Sum(ha2_sum),  
33        .Data_out_Carry(ha2_carry)  
34    );  
35  
36    assign Data_out_Sum = ha2_sum;  
37    assign Data_out_Carry = ha1_carry | ha2_carry;  
38  
39 endmodule  
40
```

Quatrus Prime Waveform

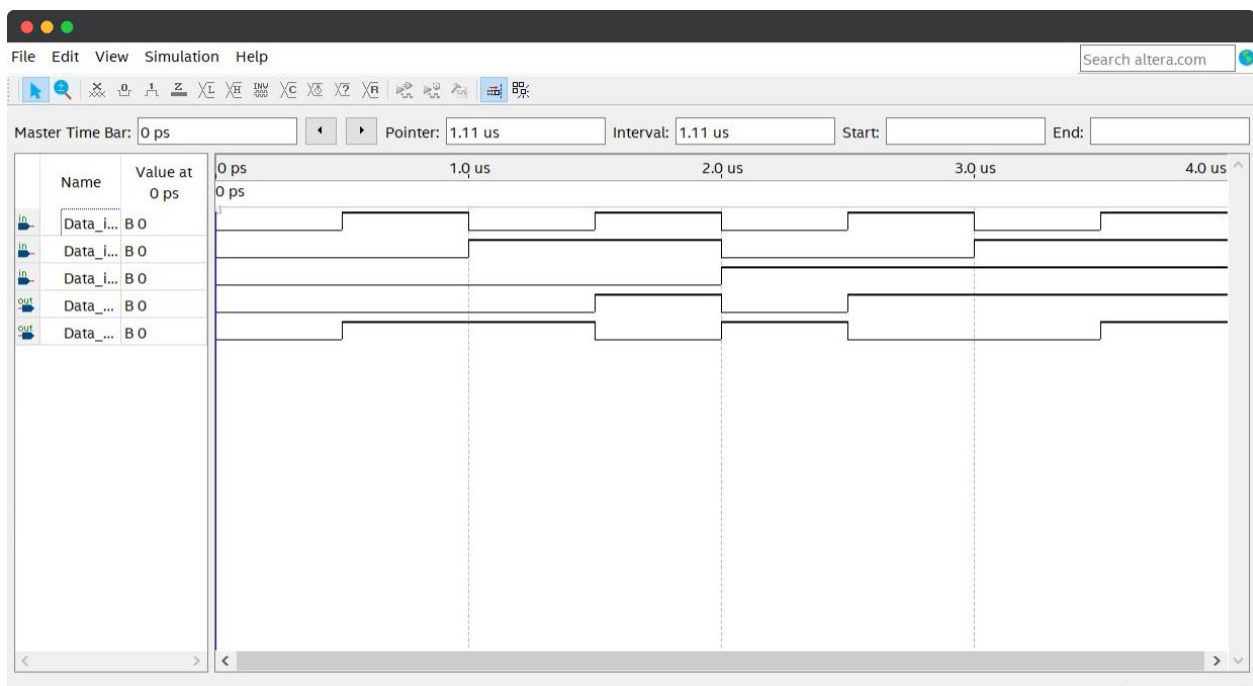

Question 4

Verilog Code

```
1 module ripple(q,w,e,r,t,y,u,i,z,x,c,v,b);
2 input q,w,e,r,t,y,u,i;
3 output z,x,c,v,b;
4 assign c0=0;
5 wire c1,c2,c3;
6 full_adder ha1(
7     .Data_in_A(q),
8     .Data_in_B(w),
9     .Data_in_C(c0),
10    .Data_out_Sum(z),
11    .Data_out_Carry(c1)
12 );
13 full_adder ha2(
14     .Data_in_A(e),
15     .Data_in_B(r),
16     .Data_in_C(c1),
17     .Data_out_Sum(x),
18     .Data_out_Carry(c2)
19 );
20 full_adder ha3(
21     .Data_in_A(t),
22     .Data_in_B(y),
23     .Data_in_C(c2),
24     .Data_out_Sum(c),
25     .Data_out_Carry(c3)
26 );
27 full_adder ha4(
28     .Data_in_A(u),
29     .Data_in_B(i),
30     .Data_in_C(c3),
31     .Data_out_Sum(v),
32     .Data_out_Carry(b)
33 );
34 endmodule
```

Quatrus Prime Waveform

